

B.Tech.
2019
2nd Sem.

JAMIA HAMDARD
Department of Food Technology
School of Interdisciplinary Science and Technology
New Delhi-110062
Examination: Even Semester 2019

Paper Name: Electrical Science

Time: 3 Hours

Note: Use of mobile phones are not allowed

Please follow proper numbering while answering the questions

Paper Code: BFTC-203


Maximum Marks: 70

SECTION A

All questions of this section are compulsory, Each question carries 5 marks

Q1) State Ohm's Law ? Explain Kirchoff's Current Law (KCL) and Kirchoff's Voltage Law (KVL) by giving examples.

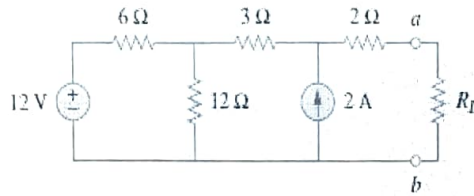Q2) State "Maximum Power Transfer Theorem". Find the value of Load Resistance (R_L) in the circuit such that maximum power transfer takes place, also find maximum power.



Q3) The voltage and current through a circuit element are-

$$v = 100 \sin(314t + 45^\circ) \text{ volts} \quad i = 100 \sin(314t + 315^\circ) \text{ amperes}$$

- (i) Identify the circuit element whether 'Inductive' or 'Capacitive' by drawing its phasor diagram and find its value also.
- (ii) Obtain expression for power.

Q4) What is a "Resonance" in an AC circuit? Draw its Phasor Diagram and also Derive the expression for Resonant Frequency in a series RLC circuit.

Q5) What is an 'Auto-Transformer'? Explain the Losses present in the transformer?


Q6) Differentiate between "Spring Control" and "Gravity Control" of Indicating Instruments.

P.T.O

SECTION B

Attempt any FOUR Questions from this section, Each question carries 10 marks

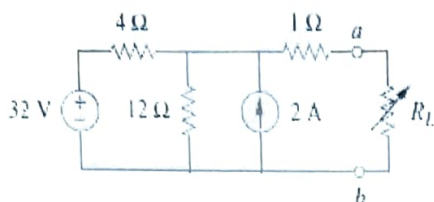Q1) State Thevenin's Theorem. Also find Thevenin's Equivalent circuit across terminals ab as shown in figure i.e find V_{th} , R_{th} and I across R_L , when $R_L = 6\ \Omega$, $16\ \Omega$ and $36\ \Omega$.



Q2) What do you mean by Bandwidth (BW) of AC circuits? Derive its expression. If the Bandwidth of a resonant circuit is 10 KHz and lower cut off frequency $f_L = 120\ \text{KHz}$, find upper cut off frequency?

Q3) Explain Principle, Construction and Working of "Attraction Type Moving Iron instruments" and "Repulsion Type Moving Iron instruments"?

Q4) Explain Permanent Magnet Type moving coil instrument? A moving coil instrument has a resistance of 2 ohm and reads upto 250 V when a resistance of 500 ohm is connected in series with it. Find current range of the instrument when it is used as an ammeter with the coil connected across a shunt resistance of 2 milliohm.

Q5) What is a "Transformer"? Explain its Principle, Construction and Working. The turns ratio of a transformer is 100/300, the primary winding is connected to a source of 3.3 kV, 50Hz supply. The load impedance ($Z_L = 110 + j45$) is connected across the secondary terminals. Calculate the following:

- (i) Value of maximum flux in the core
- (ii) Primary and secondary currents

Q6) Explain Principle, Construction and Working of a DC Generator. In case of a DC Generator, what will be the change in EMF induced, if flux is reduced by 20% and speed is increased by 20%.